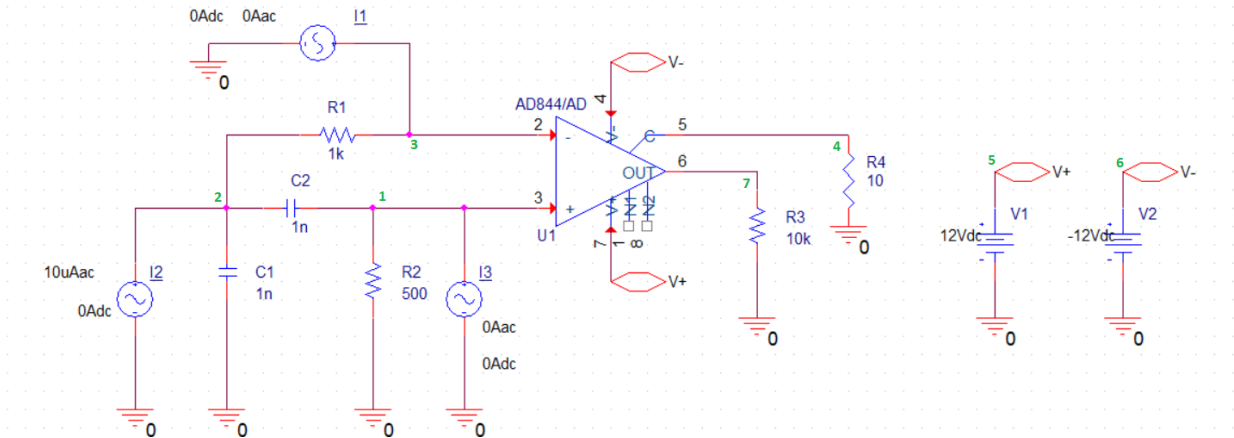


Current mode biquad using a single current conveyor (CCII+).



$$I_z = \frac{I_1(s^2 C_1 C_2 R_1 R_2 + s(C_1 + C_2)R_1 + 1) + I_2 - I_3 s C_1 R_2}{s^2 C_1 C_2 R_1 R_2 + s(C_1 + C_2)R_1 + 1}$$

Script:

*

.lib "anlg_dev.lib"

.lib "eval.lib"

X1 1 3 5 6 7 4 AD844/AD

R4 4 0 10

R2 1 0 500

R1 3 2 1k

R3 7 0 1k

c1 2 0 1n

c2 1 2 1n

v+ 5 0 DC 12

v- 0 6 DC 12

*LPF
I2 2 0 AC 10u


*BPF
*I3 1 0 AC 10u

*HPF
*I1 3 0 AC 10u
*I2 0 2 AC 10u
*I3 1 0 AC 40u


.ac oct 10 1 100MEG
.PROBE
.END

Outputs:


Lowpass

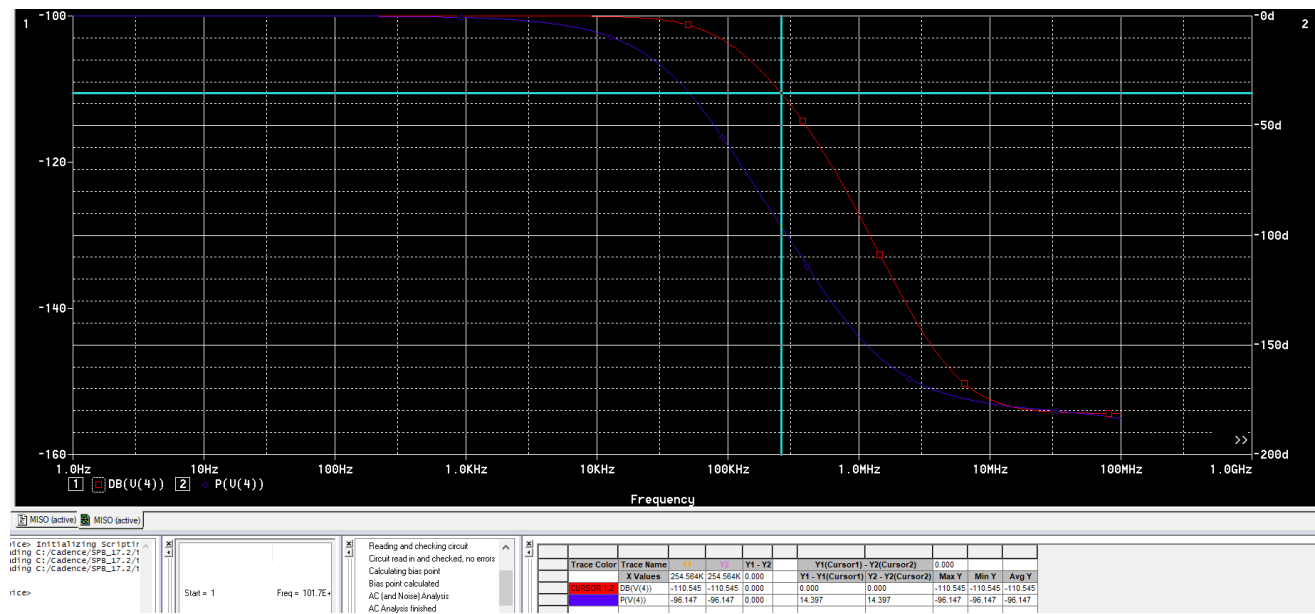


Bandpass

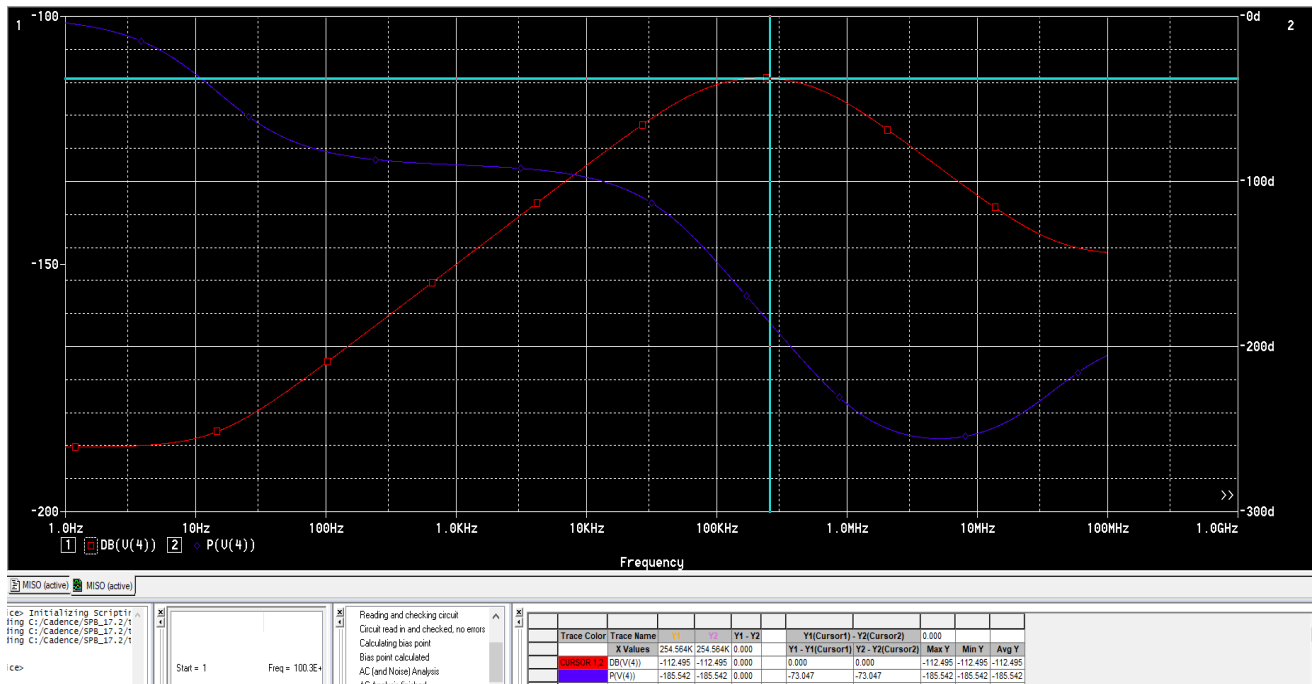

Highpass

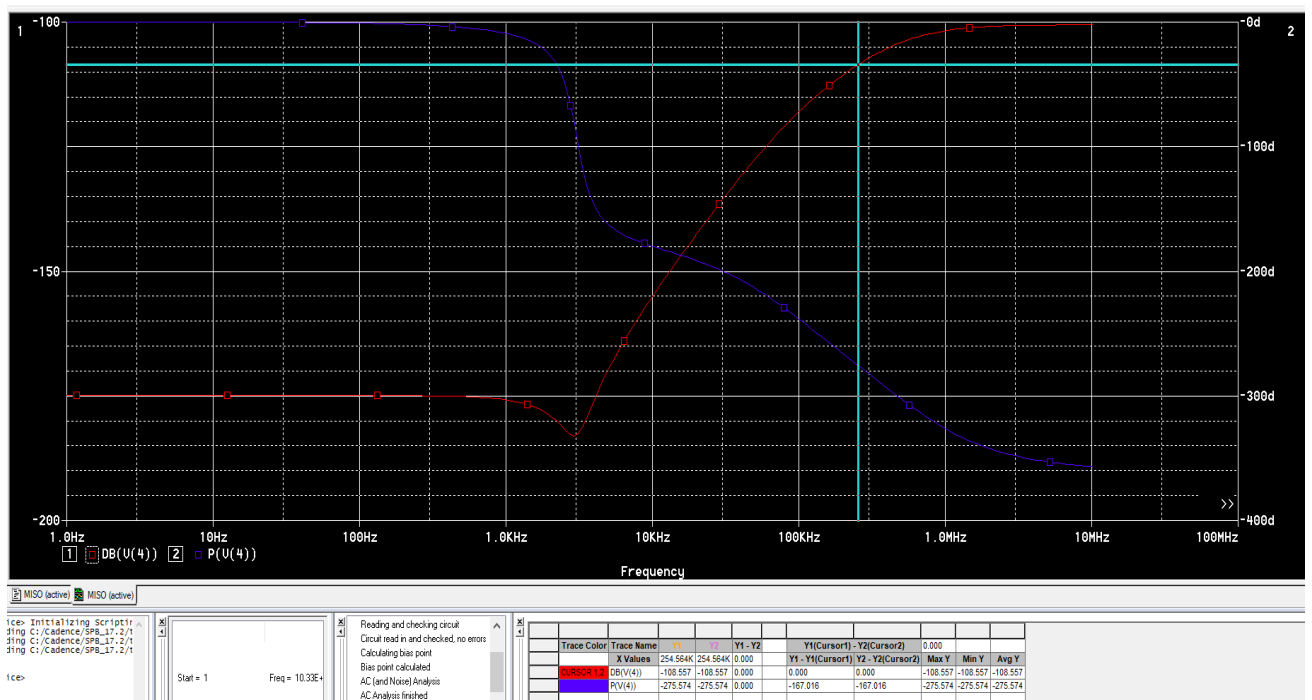

Universal biquad using CFOAs

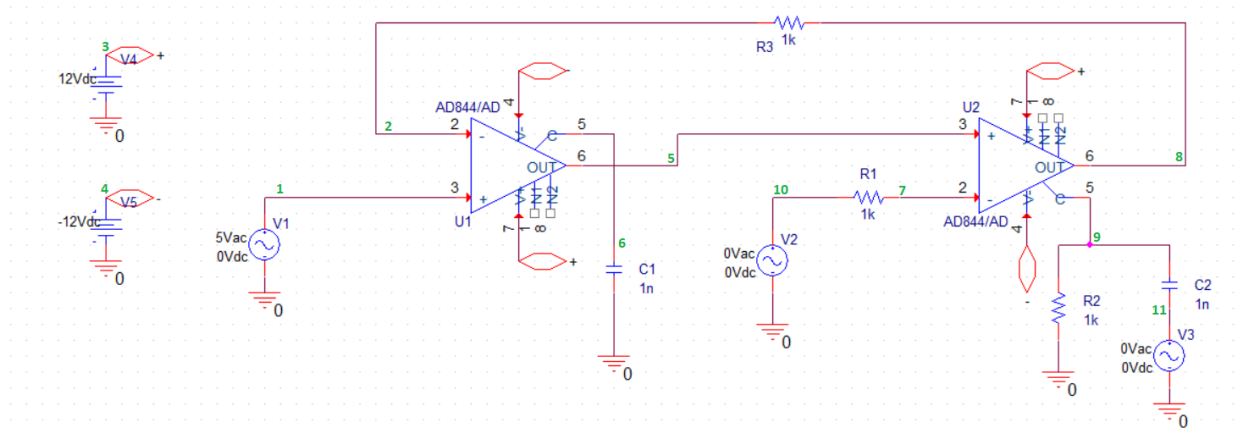

$$V_o = \frac{s^2 V_3 - \frac{s V_2}{R_1 C_2} + \frac{V_1}{C_1 C_2 R_1 R_3}}{s^2 + \frac{s}{C_2 R_2} + \frac{1}{R_1 C_1 R_3 C_2}}$$

Script:

*

.lib "anlg_dev.lib"

.lib "eval.lib"

X1 1 2 3 4 5 6 AD844/AD

X2 5 7 3 4 8 9 AD844/AD

R2 9 0 320

R1 7 10 320

R3 2 8 640

c1 6 0 2.2n

c2 9 11 2.2n

v+ 3 0 DC 12


v- 0 4 DC 12

*LPF


*V1 1 0 AC 1

```
*V2 10 0 AC 0
*V3 11 0 AC 0
*BPF
*V1 1 0 AC 0
*V2 10 0 AC 1
*V3 11 0 AC 0
*HPF
*V1 1 0 AC 0
*V2 10 0 AC 0
*V3 11 0 AC 1
*BSF
*V1 1 0 AC 1
*V2 10 0 AC 0
*V3 11 0 AC 1
*APF
V1 1 0 AC 1
V2 10 0 AC 1
V3 11 0 AC 1
.ac oct 10 10 1000MEG
.PROBE
.END
```

Output:
Lowpass

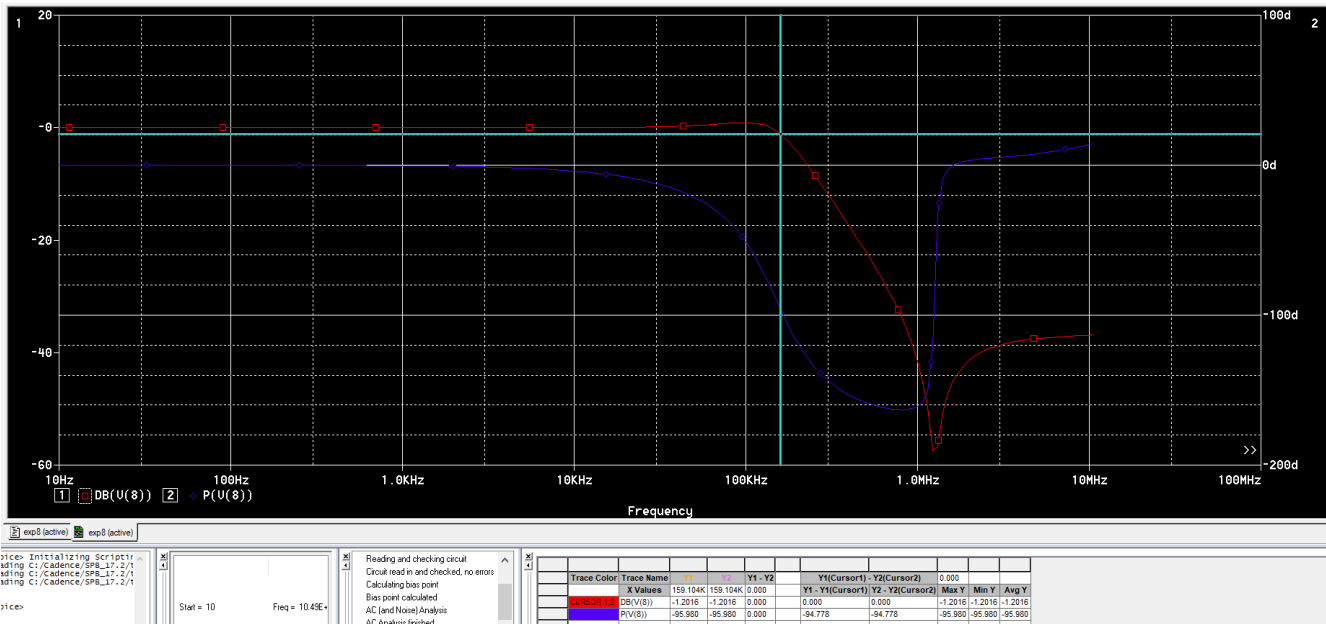

Bandpass

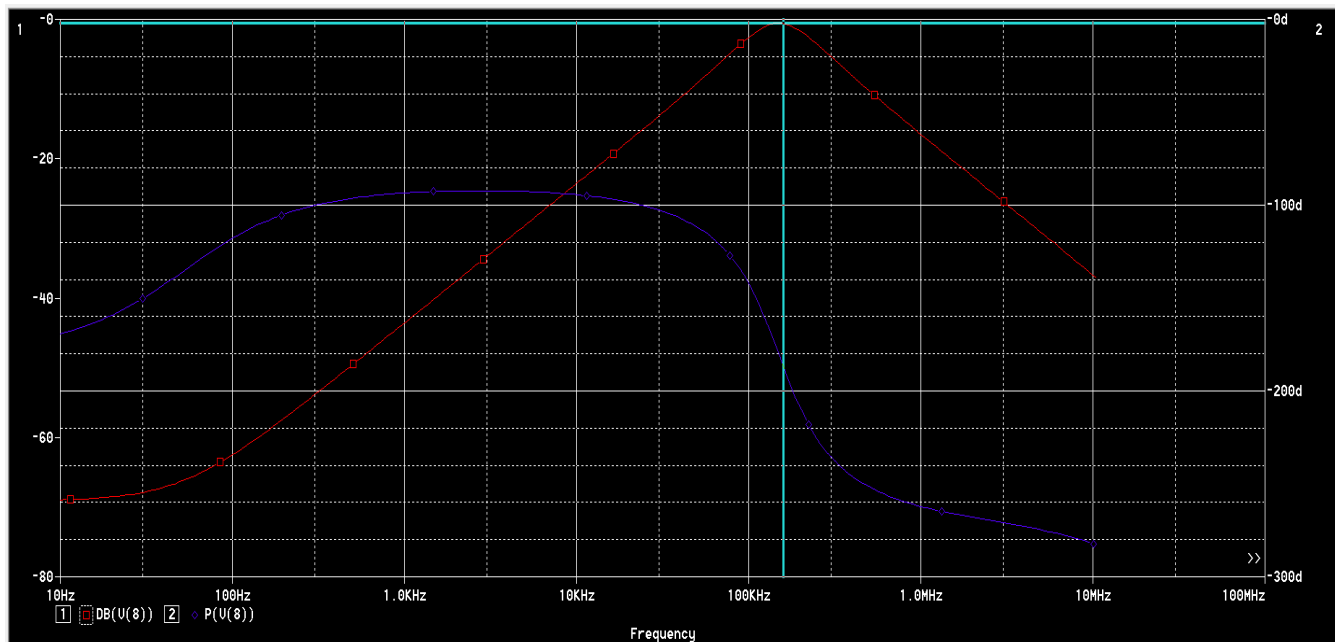

exp8 (active) exp8 (active)


ice> Initializing Scripting
ding C:/Cadence/SPB_17.2/1
ding C:/Cadence/SPB_17.2/1
ding C:/Cadence/SPB_17.2/1

Start = 10 Freq = 10.45E+

Reading and checking circuit
Circuit read in and checked, no errors
Calculating bias point
Bias point calculated
AC (and Noise) Analysis
AC Analysis finished

Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	Max Y	Min Y	Avg Y
Red	DB(U(8))	-588.966m	-588.966m	0.000	0.000	-588.966m	-588.966m	-588.966m
Blue	P(U(8))	-186.935	-186.935	0.000	-186.346	-186.935	-186.935	-186.935

Highpass

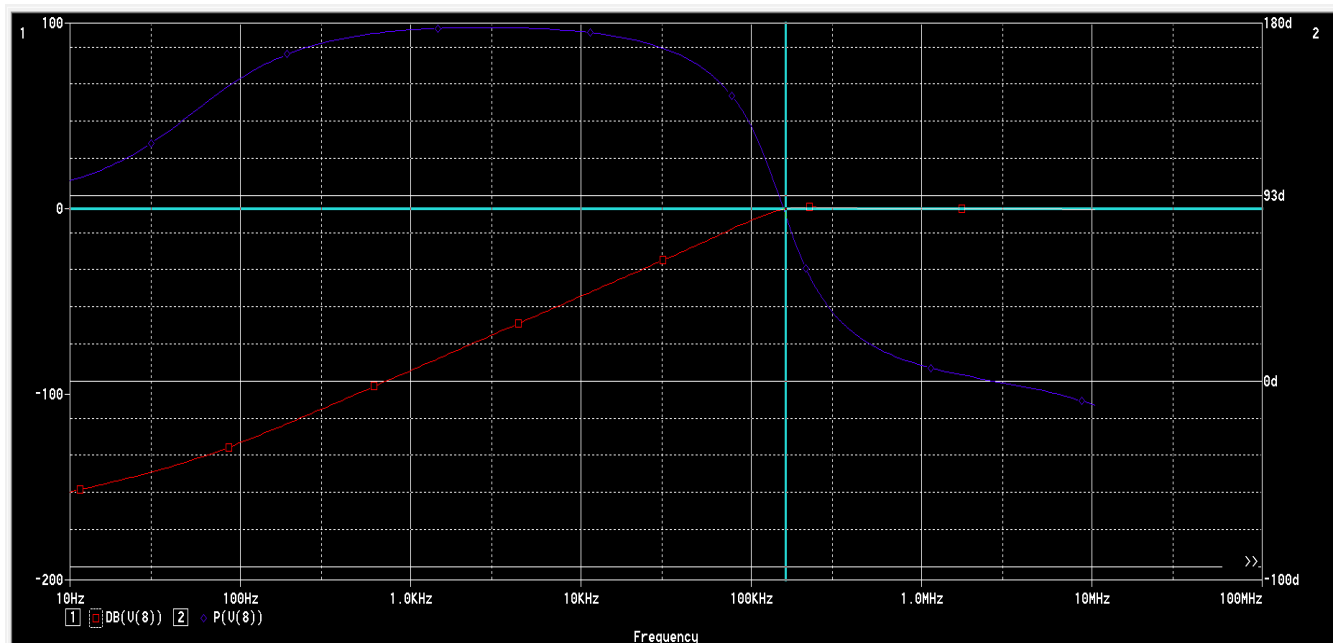

exp8 (active) exp8 (active)


ice> Initializing Scripting
ding C:/Cadence/SPB_17.2/1
ding C:/Cadence/SPB_17.2/1
ding C:/Cadence/SPB_17.2/1

Start = 10 Freq = 10.45E+

Reading and checking circuit
Circuit read in and checked, no errors
Calculating bias point
Bias point calculated
AC (and Noise) Analysis
AC Analysis finished
Tried with time domain Solver 11 =

Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	Max Y	Min Y	Avg Y
Red	DB(U(8))	-154.365m	-154.365m	0.000	0.000	-154.365m	-154.365m	-154.365m
Blue	P(U(8))	82.915	82.915	0.000	83.069	82.915	82.915	82.915

Bandstop

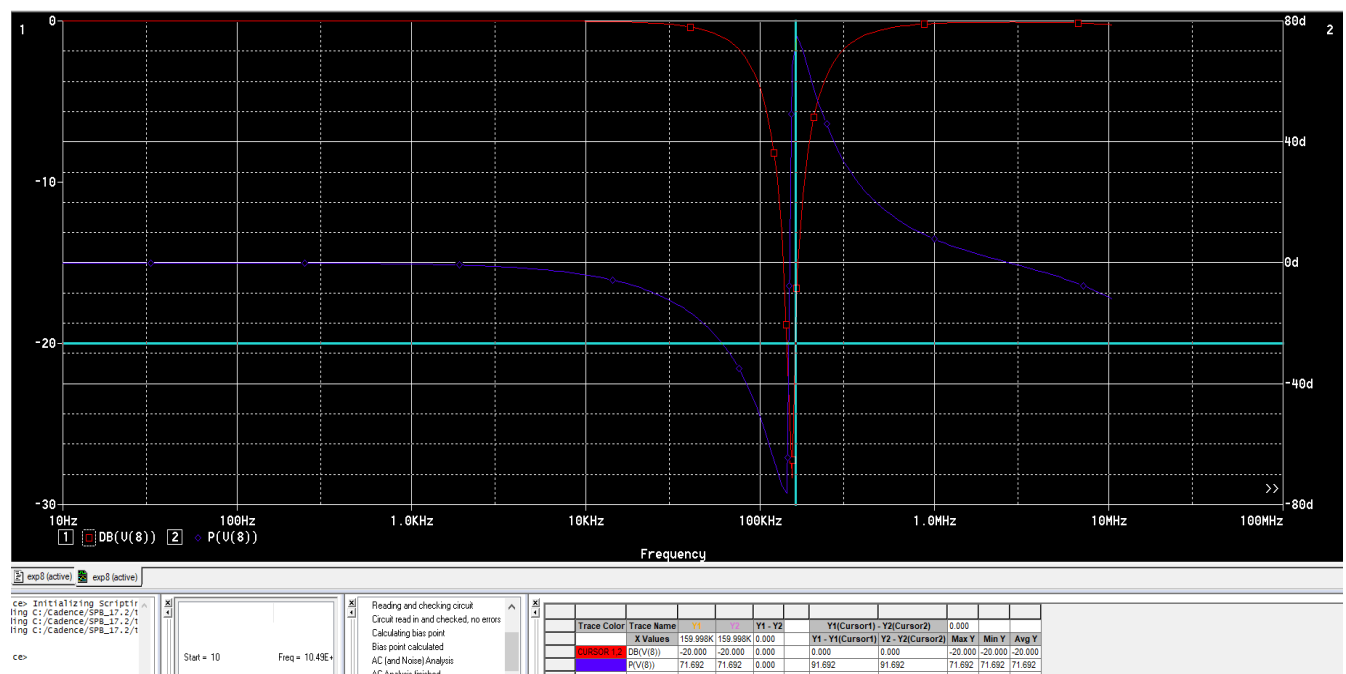

Allpass

