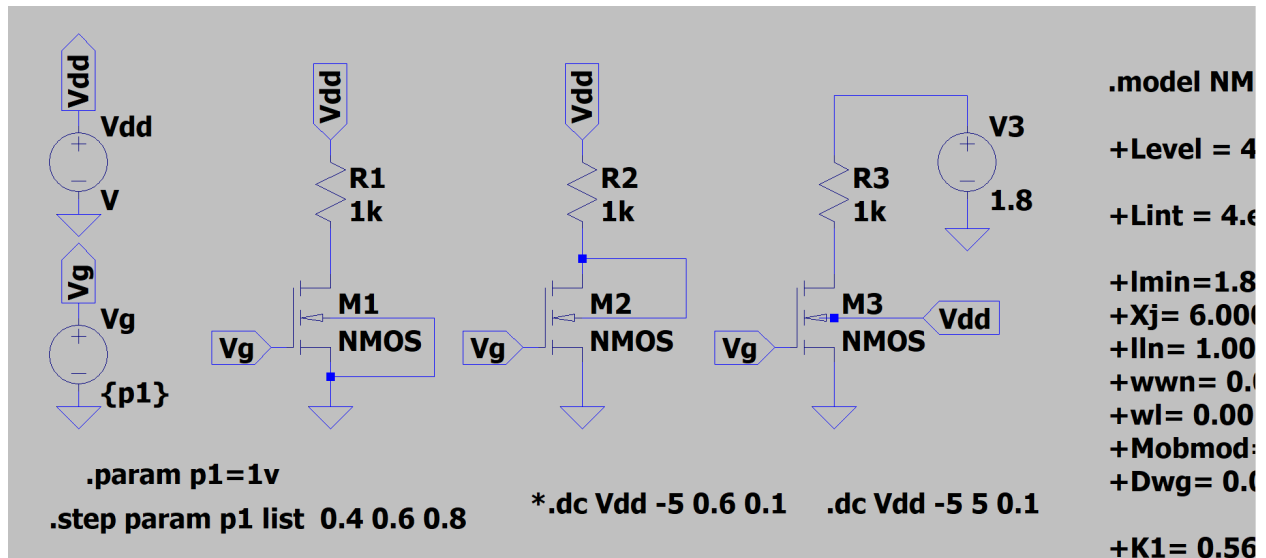



## Schematic:





## Outputs:

W=1u, L=0.27u

### 1. NMOS Common source amplifier

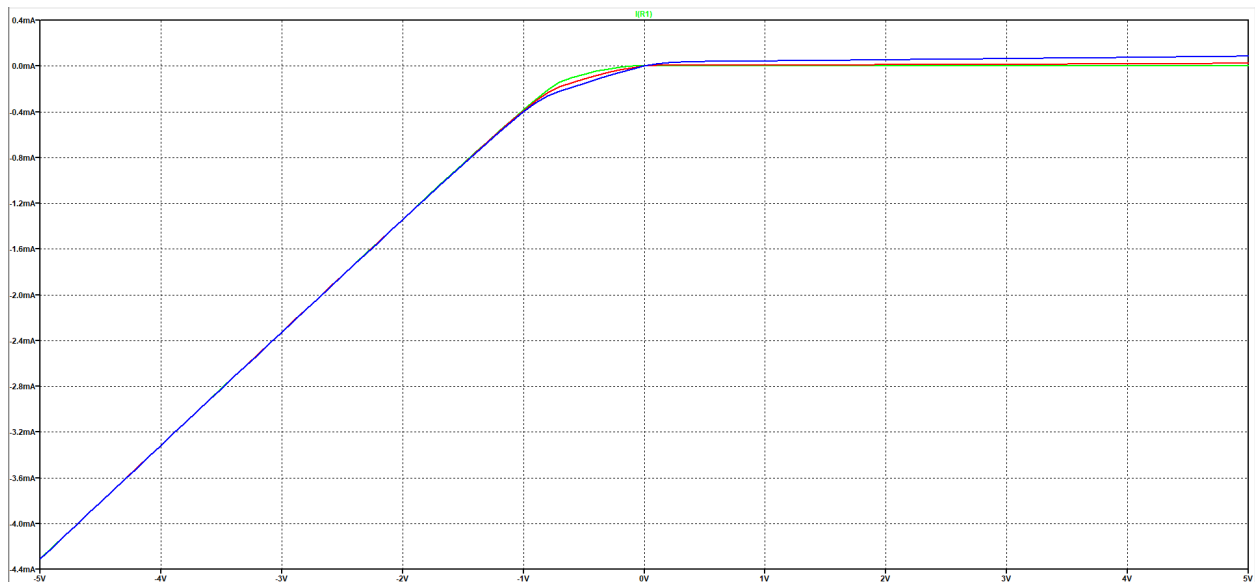
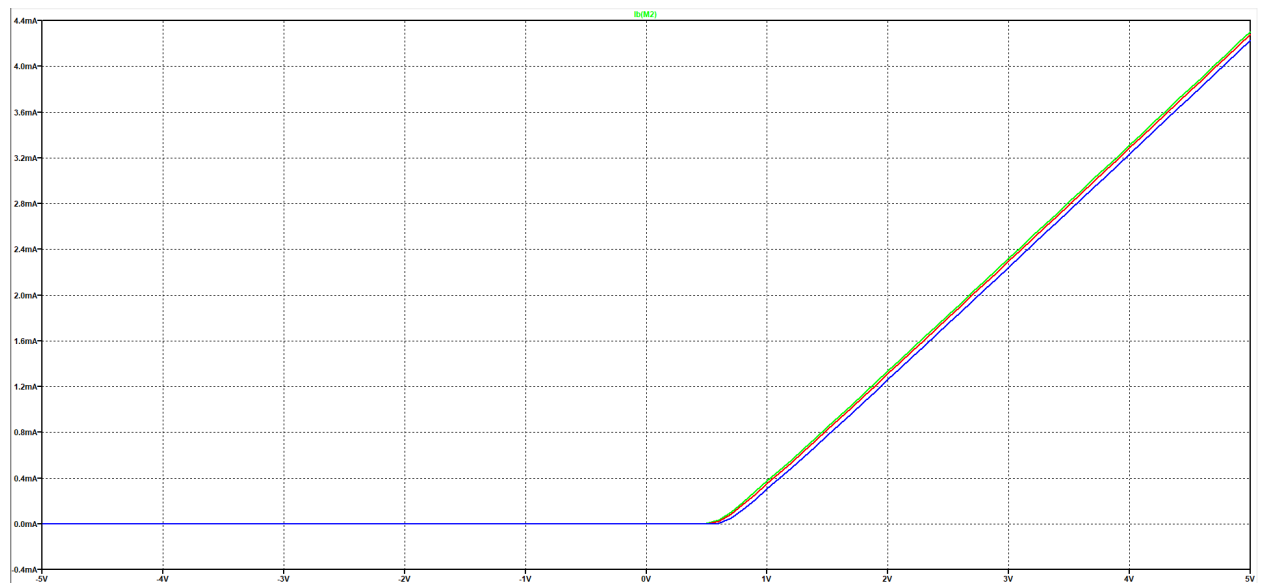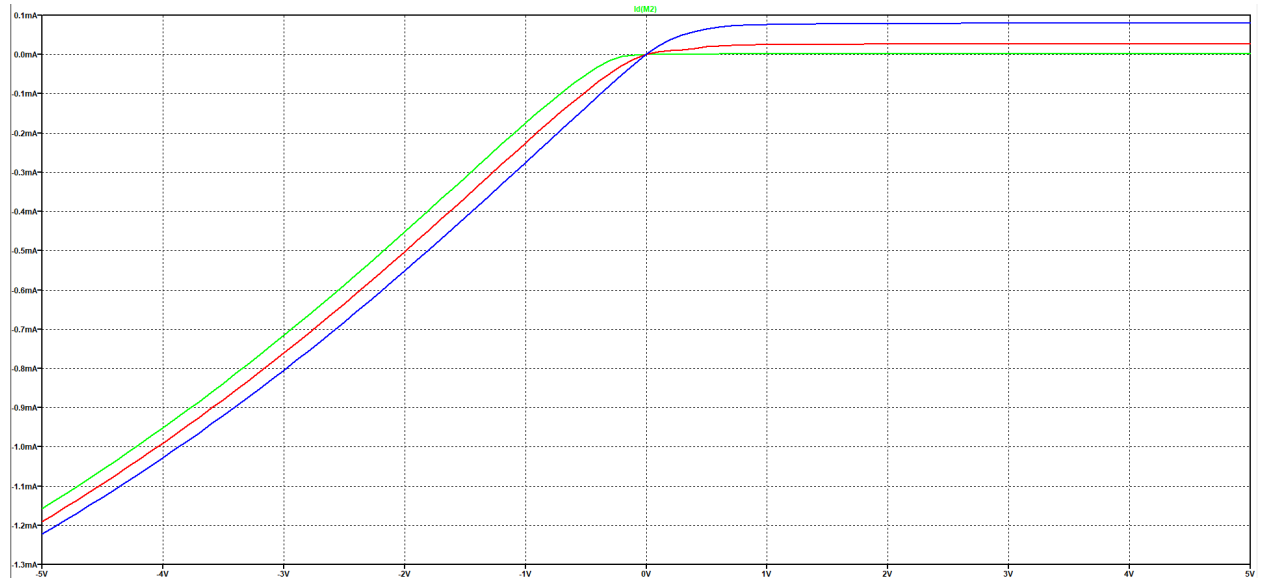
### 2. Bulk-driven MOSFET with bulk shorted with drain



3. Bulk driven MOS with bulk provided with a dc sweep -5v to .6 volt.

